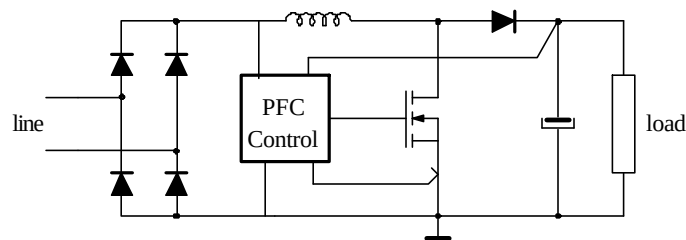


Active PFC Boost Rectifier

Power section



CHARACTERISTICS:


Input voltage: $V_{in} = 90\text{-}260V_{RMS}$
Output voltage: $V_o = 380V$
Output power: $P_o = 600W$
Switching frequency: $f_s = 70kHz$

VALUES:

Output capacitor: $C = 680 \mu F$
Inductor: $L = 600 \mu H$
Mosfet: IRFP450
Diode: RURP1560
Controller: L4981A

Active PFC Boost Rectifier

Power section and related EMI aspects

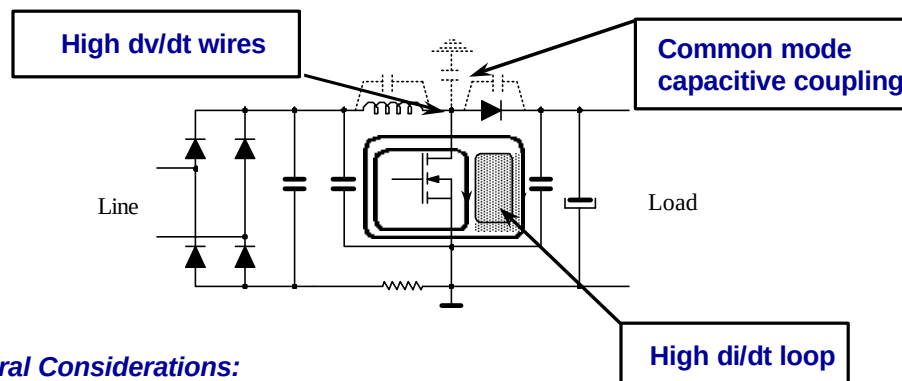

General Considerations:


MOSFET and DIODE are the main noise generators

- Short wires where high dv/dt
- Small area of fast di/dt loops
- Short paths for return currents

Careful Layout

Circuit Layout (components)

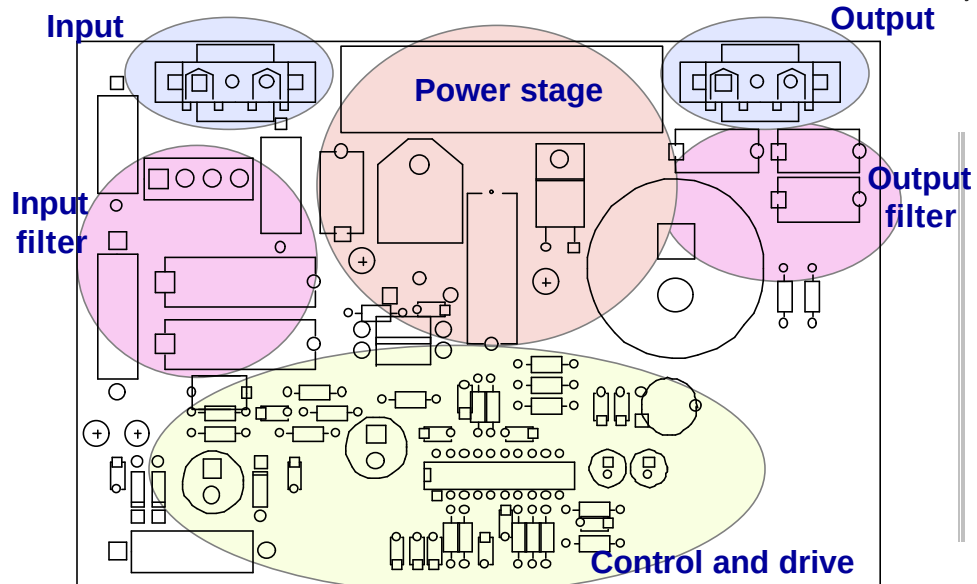
Giorgio Spiazzi
University of Padova
Italy



Active PFC Boost Rectifier

Circuit Layout (solder layer)

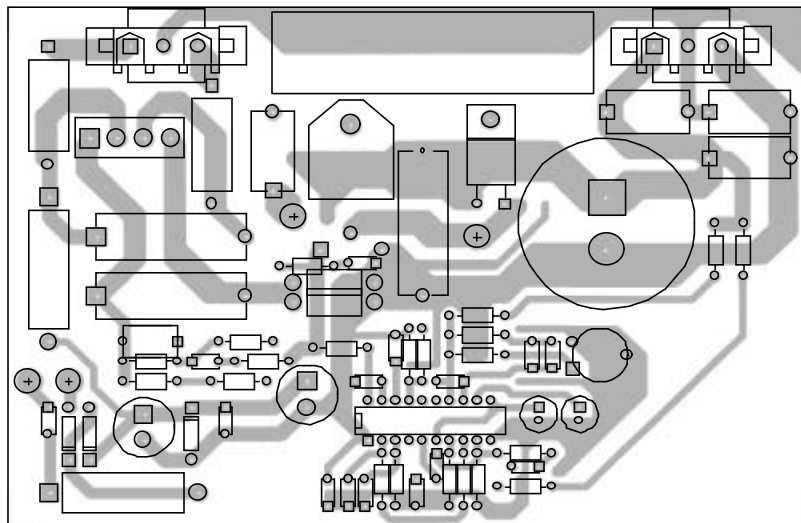
Giorgio Spiazzi
University of Padova
Italy



Active PFC Boost Rectifier

Giorgio Spiazzi
University of Padova
Italy


Circuit Layout (component layer)

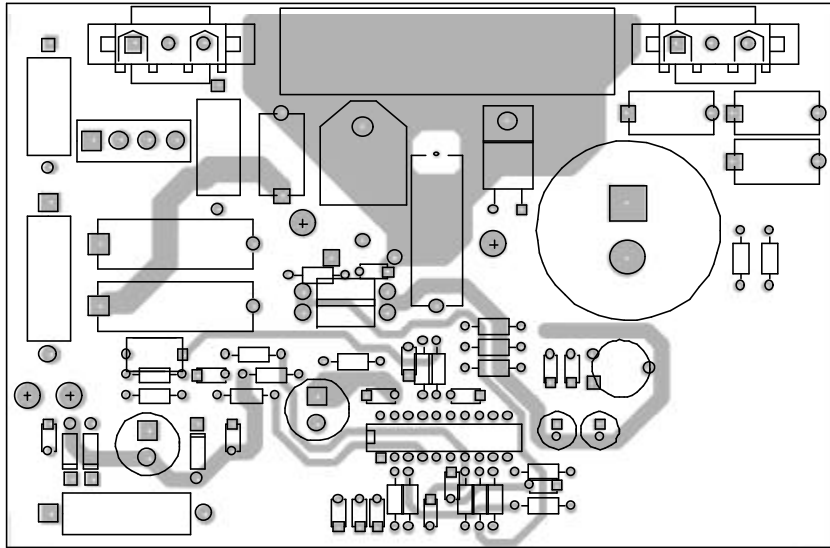

Active PFC Boost Rectifier

Giorgio Spiazzi
University of Padova
Italy


Circuit Layout Considerations

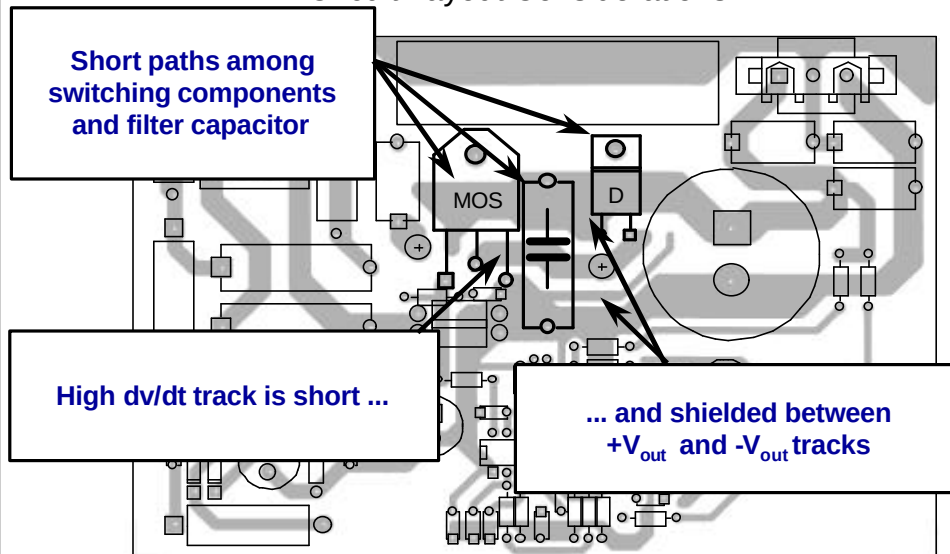

Active PFC Boost Rectifier

Circuit Layout Considerations

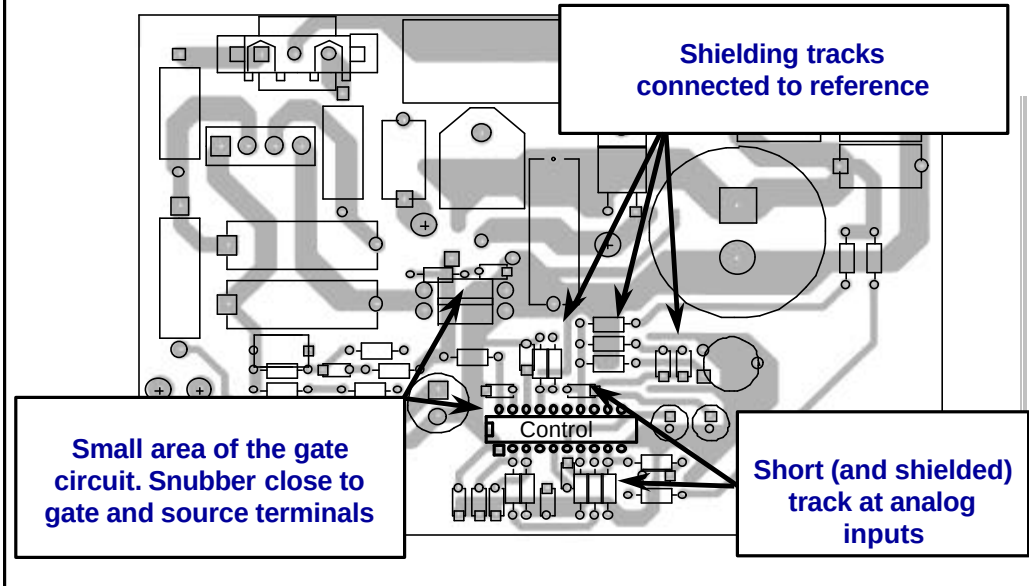
Giorgio Spiazzi
University of Padova
Italy



Active PFC Boost Rectifier

Circuit Layout Considerations

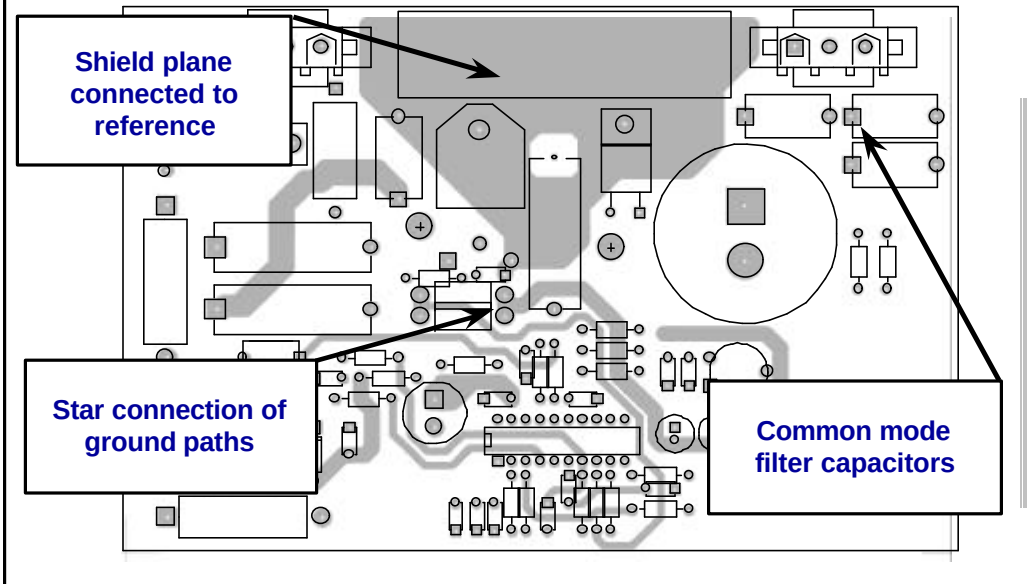Giorgio Spiazzi
University of Padova
Italy




Active PFC Boost Rectifier

Power section with EMI Filters


High CM impedance

Low CM impedance

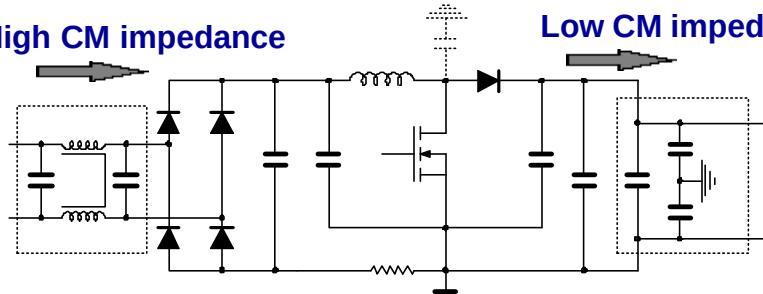

Coupled inductors show high common mode inductance but low differential mode inductance:

Ex: 6.8 mH CM, 70 μH DM

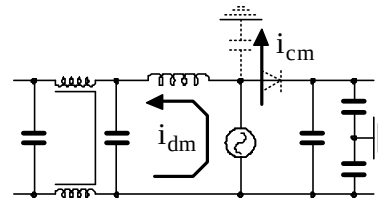

Active PFC Boost Rectifier


Input filter design - Differential Mode

Ripple amplitude

$$\Delta I_{\max} = \frac{U_{\text{out}}}{8 f_s L} \cong 1.13 \text{ A}$$

triangular waveform

Differential mode input noise:	70 kHz,	87 dB μV
(peak values)	140 kHz,	57 dB μV
	210 kHz,	40 dB μV
	280 kHz,	26 dB μV
	350 kHz,	19 dB μV
	420 kHz,	9 dB μV

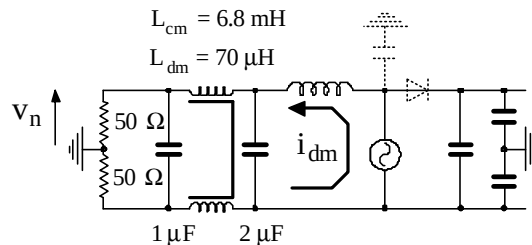


a suitable margin (20 dB μV) is maintained for the common mode noise and possible resonances

Active PFC Boost Rectifier

Input filter design - Common Mode

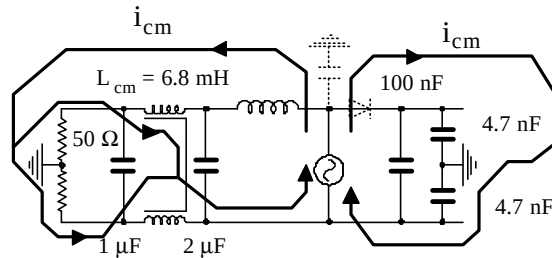Giorgio Spiazzi
University of Padova
Italy




- Several current return paths are present
- The main one is on the output side of the PFC
- High value of filter inductor reduces current term at the input side
- CM input side current generates DM input noise due to asymmetrical converter topology
- Adding CM capacitors at the input side reduces input CM voltage noise but the increased CM current causes additional DM noise

Prototype Tests

Input behavior

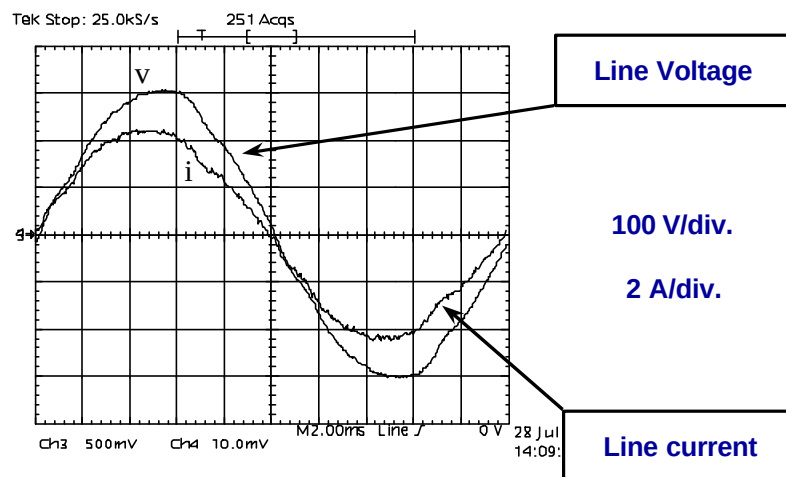
Giorgio Spiazzi
University of Padova
Italy



Prototype Tests

Giorgio Spiazzi
University of Padova
Italy

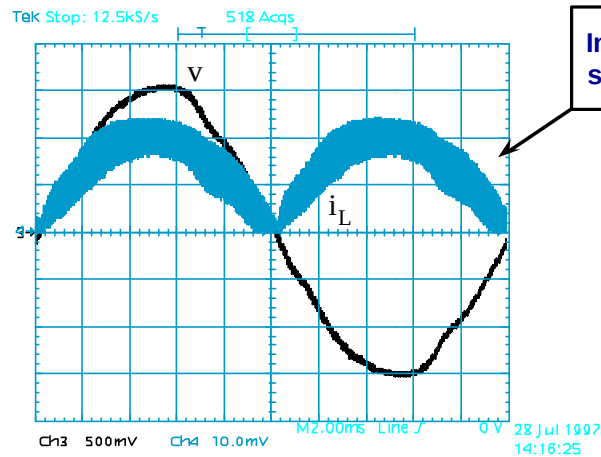Line Voltage and Inductor Current
(peak to peak sampling)





Inductor current
switching ripple

Prototype Tests



Giorgio Spiazzi
University of Padova
Italy

Gate drive circuit

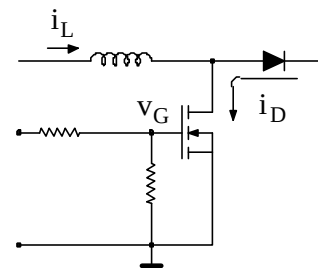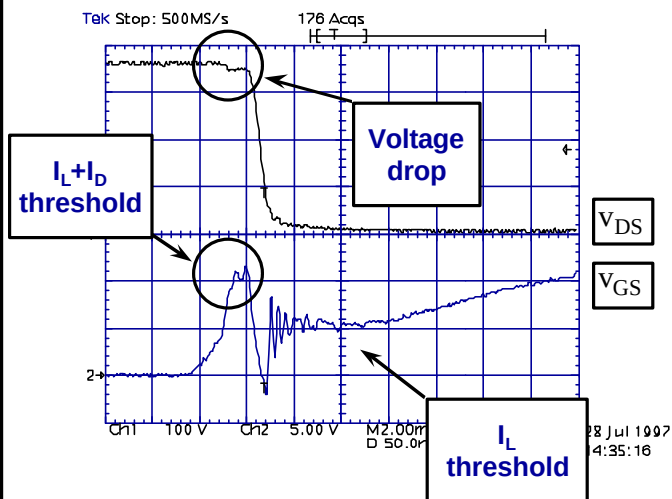

Prototype Tests



Gate drive circuit

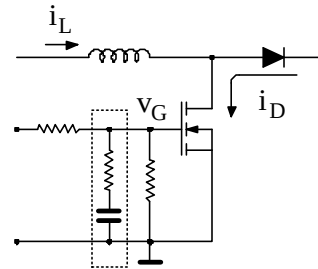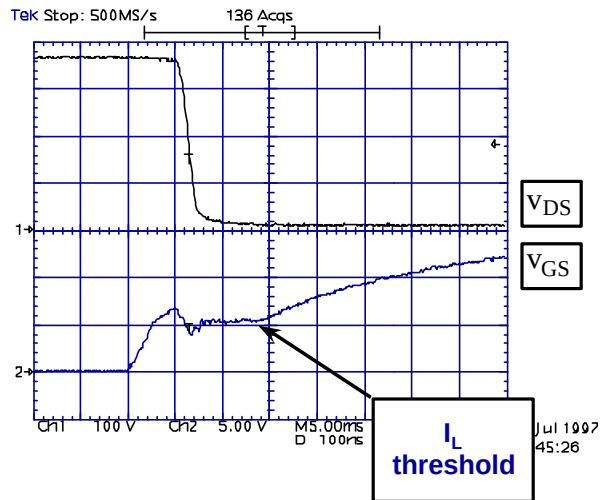

Commutation is slowed-down

Prototype Tests



Gate drive circuit

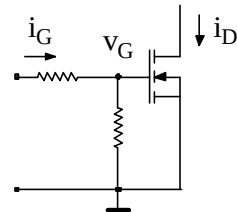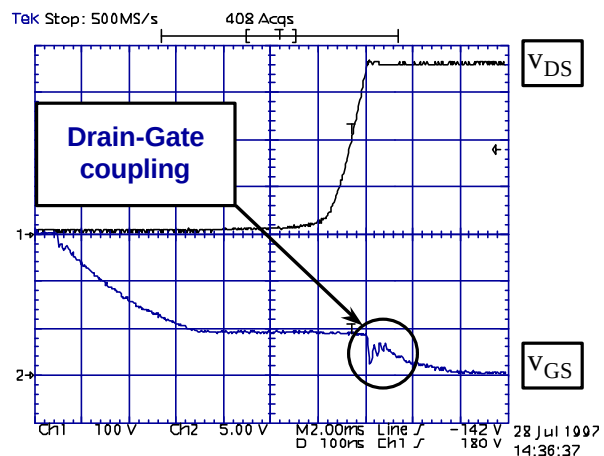

Prototype Tests

Giorgio Spiazzi
University of Padova
Italy


Gate drive circuit

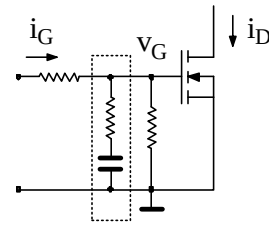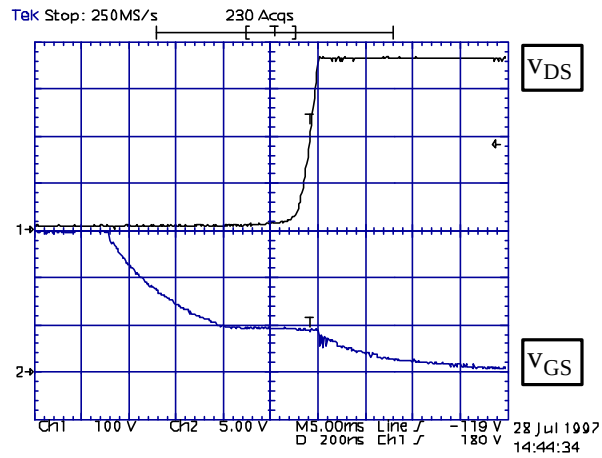

Prototype Tests

Giorgio Spiazzi
University of Padova
Italy

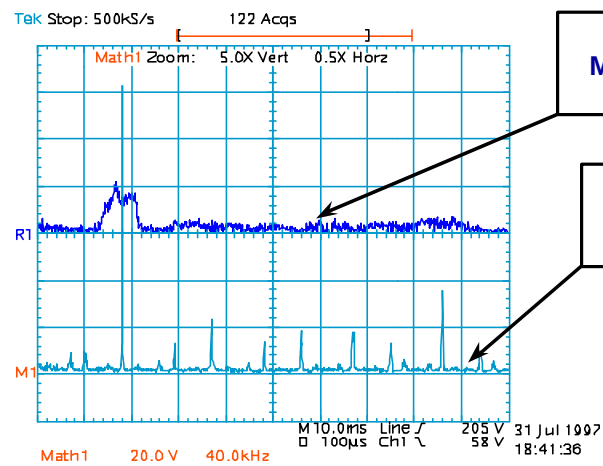Modulation of Switching Frequency V_{DS} Spectra





Modulated

Fixed

Prototype EMI Tests

Conducted noise (peak measure)

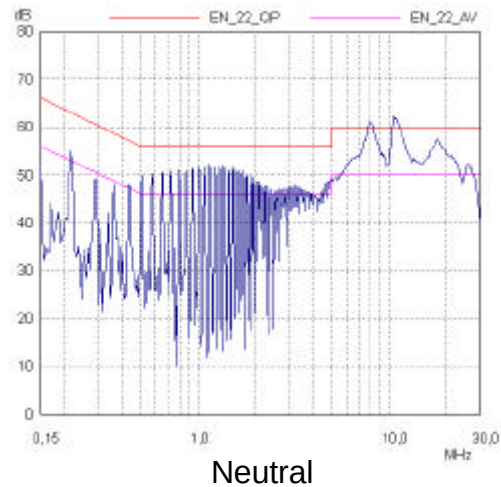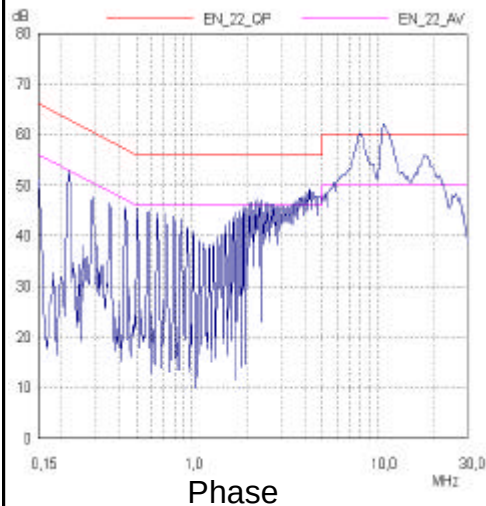Giorgio Spiazzi
University of Padova
Italy





Prototype EMI Tests

Conducted noise (peak measure)

Giorgio Spiazzi
University of Padova
Italy

Introducing input-side common-mode filter capacitors

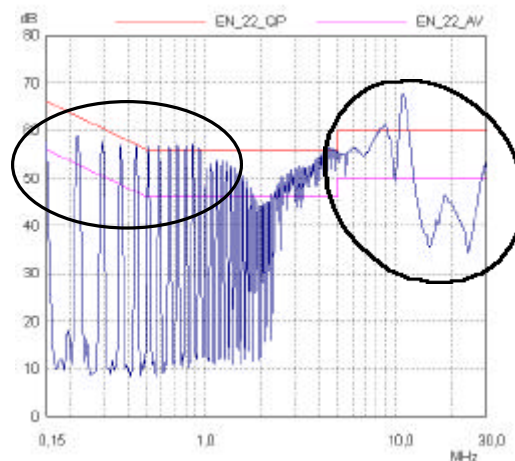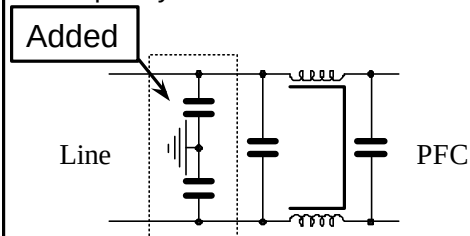- Differential noise increases (*circuit is not symmetrical*) and low-frequency behavior is worse
- A resonance, between input and output CM filter capacitors and the inductances of their connections, appears, modifying the high-frequency behavior





Prototype EMI Tests

Giorgio Spiazzi
University of Padova
Italy

Conducted noise (peak measure)

Increased output-side common-mode capacitors

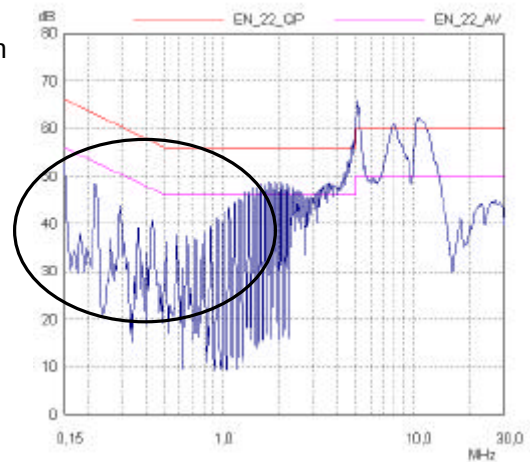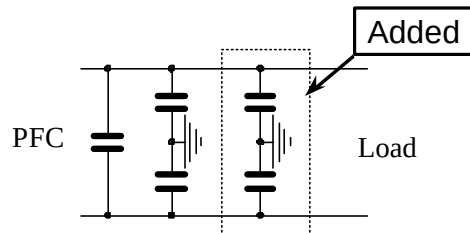- Common mode currents are closed on the output side (*no additional voltage drop on the input filter occurs*)
- Low-frequency behavior is improved
- High-frequency behavior becomes worse due to resonance of two CM filter capacitors and their connections





Prototype EMI Tests

Giorgio Spiazzi
University of Padova
Italy

Conducted noise (peak measure)

By connecting the heatsink to the negative rail (*capacitive currents are closed "near" to the Mosfet source*):

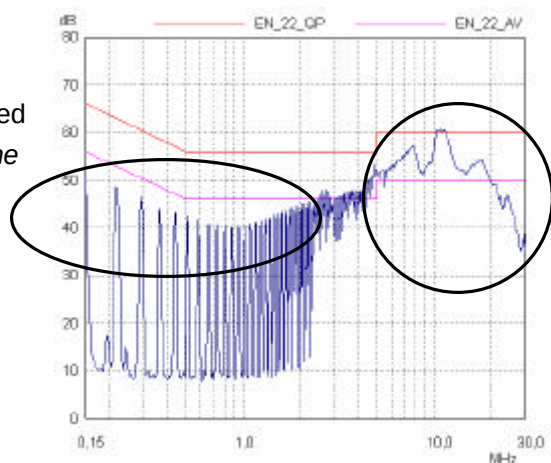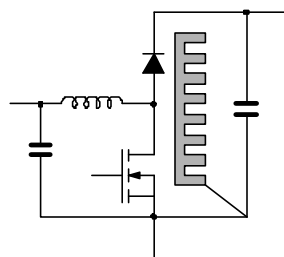- Low-frequency behaviour is improved
- High-frequency behavior is good (*the heatsink shields all circuitry*)





Prototype EMI Tests

Conducted noise (peak measure)

Giorgio Spiazzi
University of Padova
Italy

By inserting a shield, between Mosfet and heatsink, connected to Mosfet source (*drain coupled capacitive currents are closed directly to the Mosfet source*)

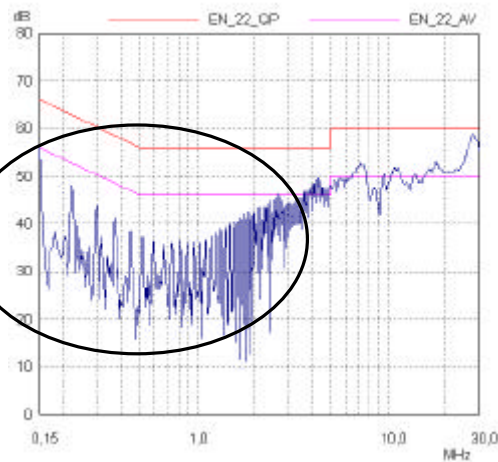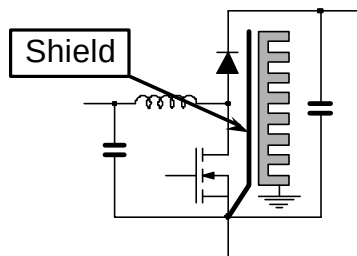- Low-frequency behavior is improved (*common mode noise is reduced*)
- High-frequency behavior is good (*Using the heatsink as shield of the whole circuit gives however better results*)



Prototype EMI Tests

Conducted noise (peak measure)

Giorgio Spiazzi
University of Padova
Italy


Switching Frequency Modulation

Switching frequency harmonic components disappear

- Measured peak noise remains unchanged
- Measured average noise is considerably reduced

Peak

Average

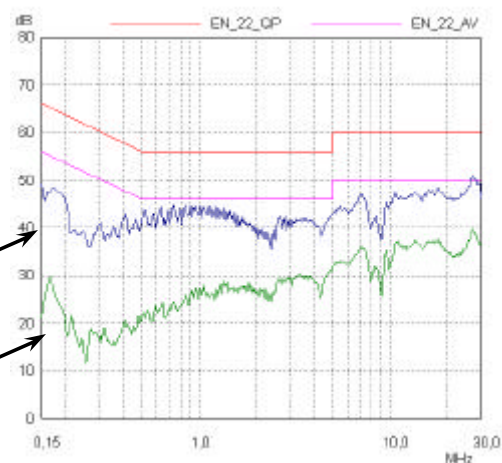



Prototype EMI Tests

Giorgio Spiazzi
University of Padova
Italy

Conducted noise (peak measure)

Effect of Diode Reverse Recovery (Disconnecting gate snubber)

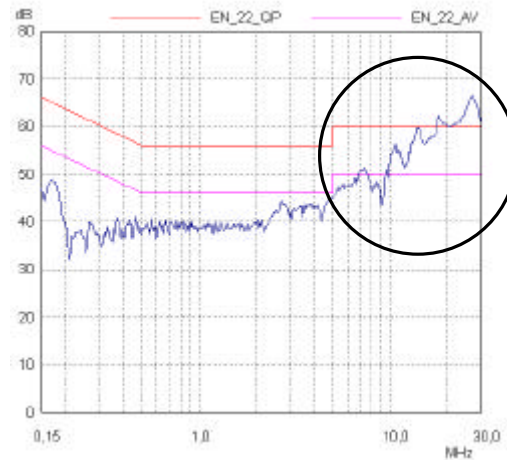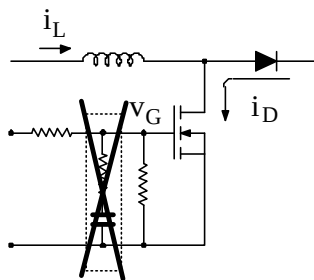- Low-frequency behavior is almost unchanged
- High-frequency behavior is heavily worsened





Prototype EMI Tests

Giorgio Spiazzi
University of Padova
Italy

Conducted noise (peak measure)

Increasing gate resistor

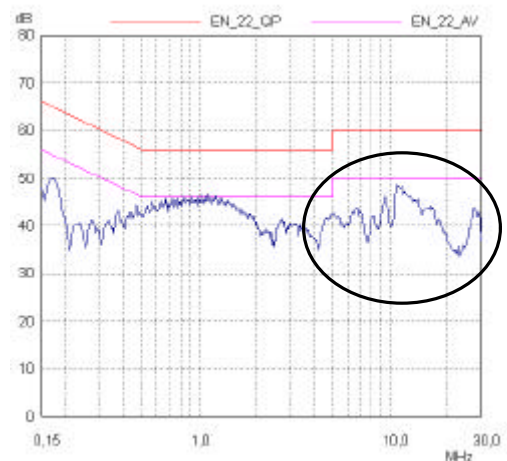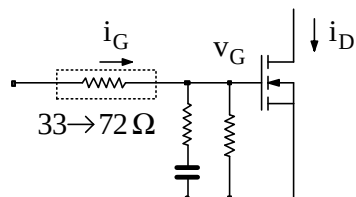- Low-frequency behavior remains unchanged
- High-frequency behavior is improved (MOSFET commutation slows down)



Prototype EMI Tests

Giorgio Spiazzi
University of Padova
Italy

By spreading the ac wires close to the input filter (filter inductors inside plastic can)

- Low-frequency behavior becomes worse (*input wires capture leakage magnetic field of filter inductor*)
- High-frequency behavior remains unchanged

